

Jin-Soo Kim  
(jinsoo.kim@snu.ac.kr)

Systems Software &  
Architecture Lab.  
Seoul National University

Fall 2019

# Logic Design

Chap. 4.2, Appendix A




# Logic Design Basics

- Information encoded in binary
  - Low voltage = 0, High voltage = 1
  - One wire per bit
  - Multi-bit data encoded on multi-wire buses
- Combinational elements
  - Operate on data
  - Output is a function of input
- State (sequential) elements
  - Store information

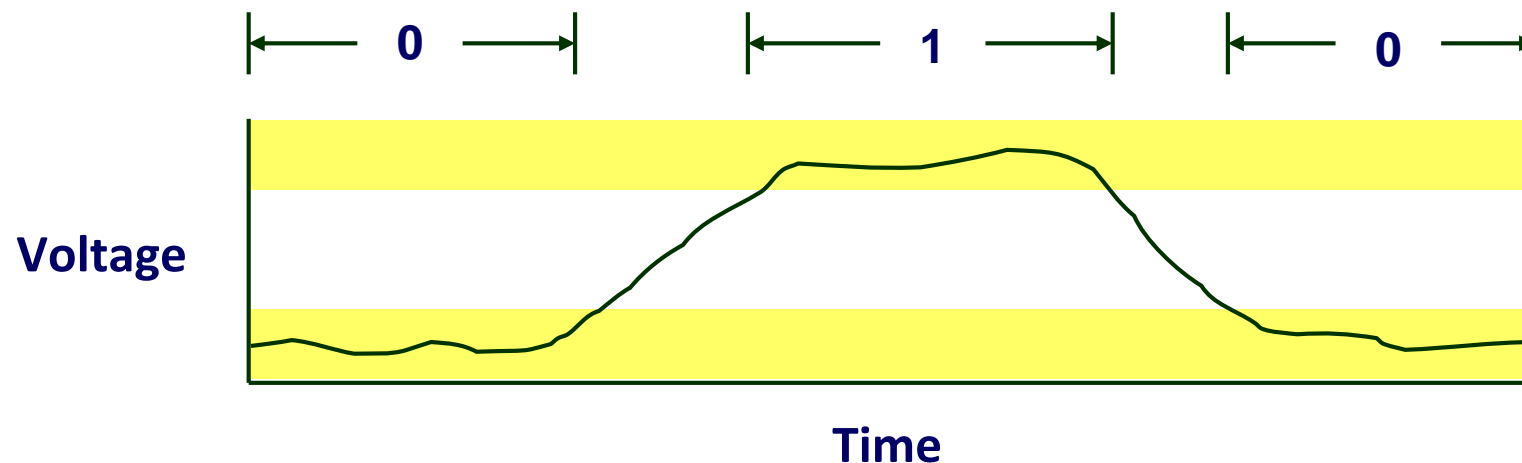
# Digital Signals

- Use voltage thresholds to extract discrete values from continuous signal
- Simplest version: 1-bit signal
  - Either high range (1) or low range (0)
  - With guard range between them
- Not strongly affected by noise or low quality circuit elements
  - Can make circuits simple, small, fast, and robust






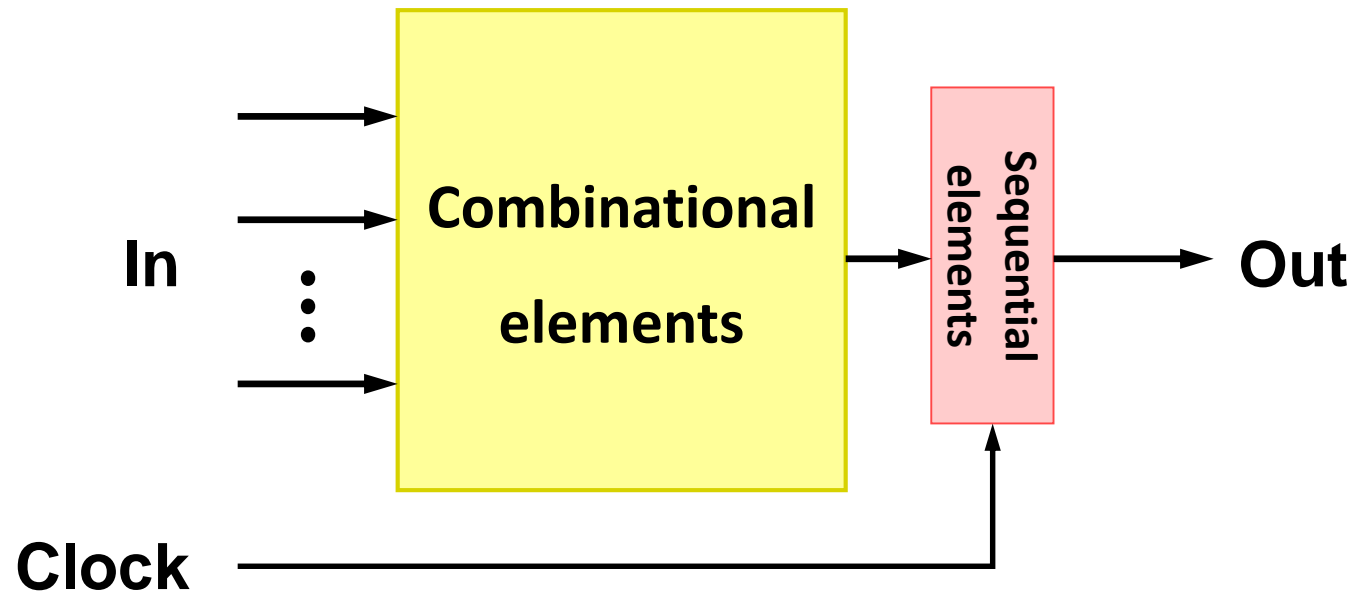
# Digital Systems

- Three components required to implement a digital system
  - **Combinational elements** to compute Boolean functions
  - **Sequential elements** to store bits
  - **Clock signals** to regulate the updating of the memory elements



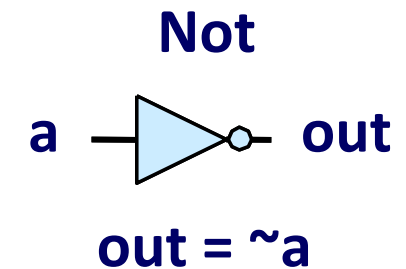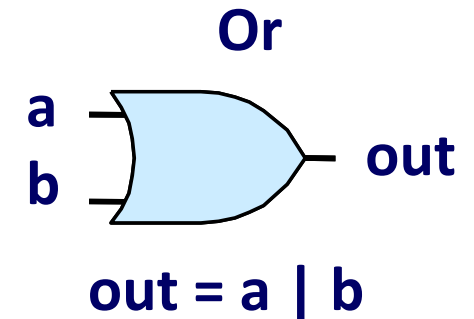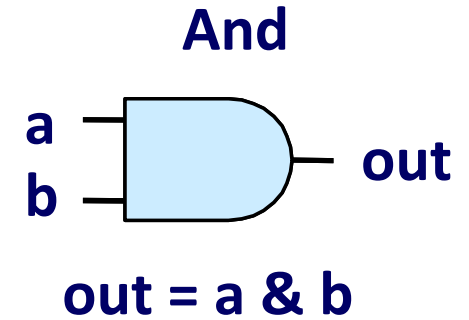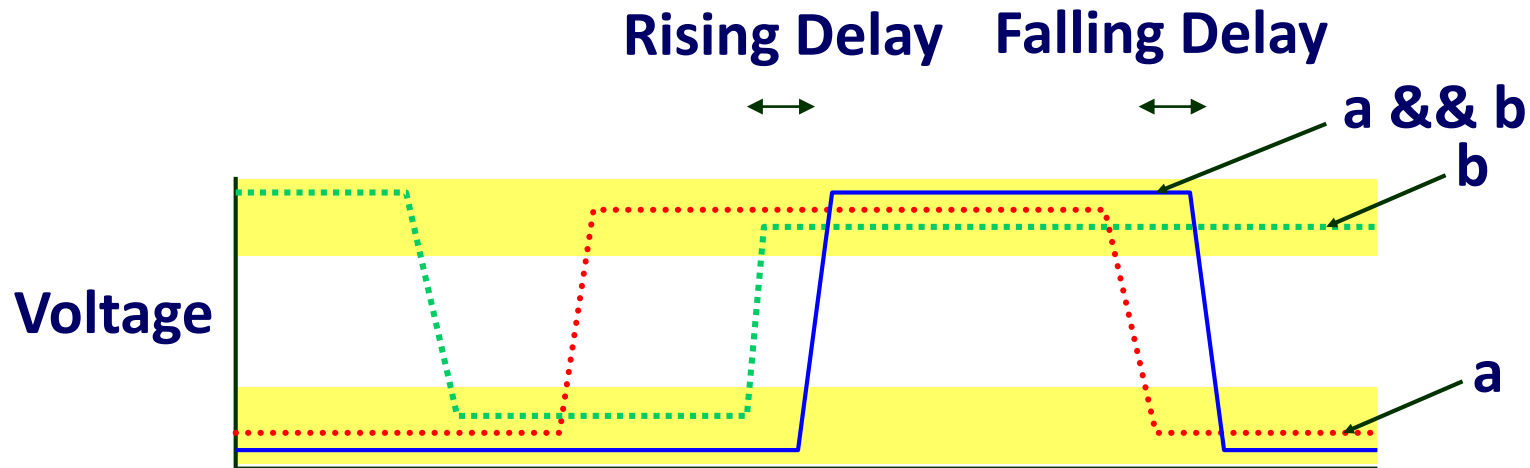
# Computing with Logic Gates

- Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs (with some, small delay)


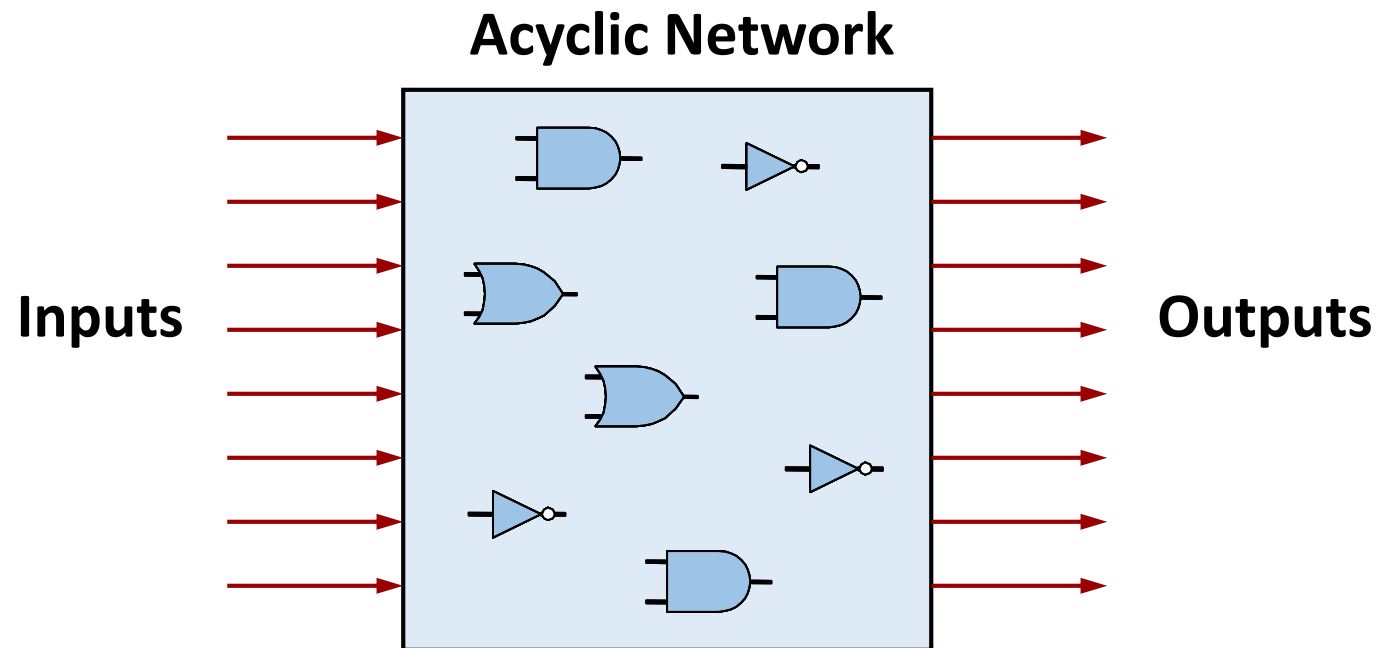
# Combinational Circuits


- Acyclic network of logic gates
  - Continuously responds to changes on primary inputs
  - Primary outputs become (after some delay) Boolean functions of primary inputs



# Combinational Elements: Examples


## ■ AND-gate

- $Y = A \& B$

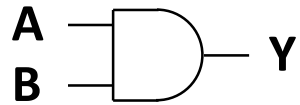


## ■ Adder

- $Y = A + B$

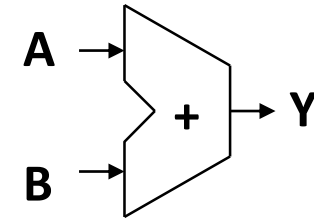


## ■ Multiplexer

- $Y = S? A : B$

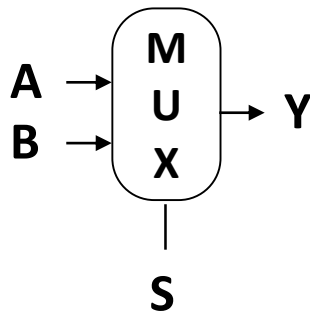


## ■ Arithmetic/Logic Unit

- $Y = F(A, B)$



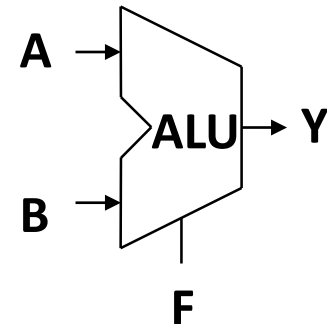


# Sequential Elements: Examples

- Flip-flops

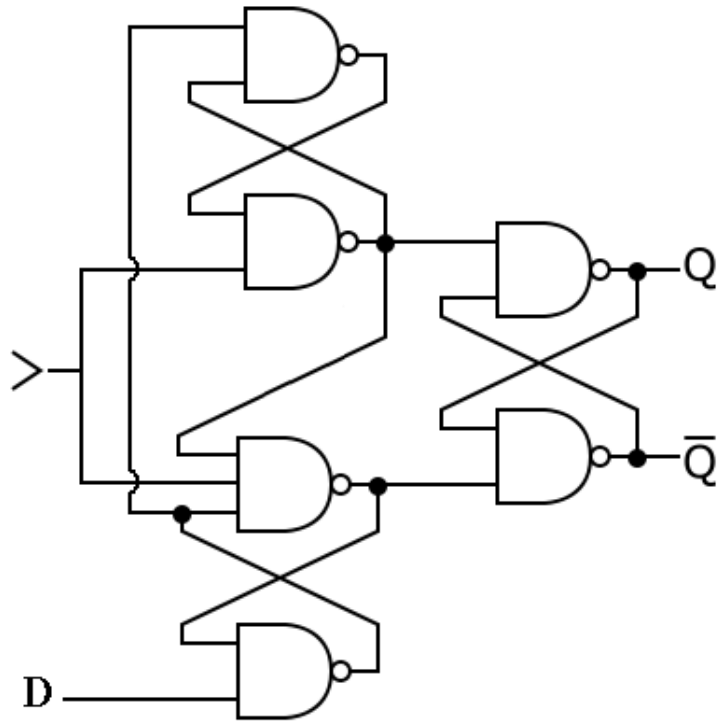



Edge-triggered D flip-flop

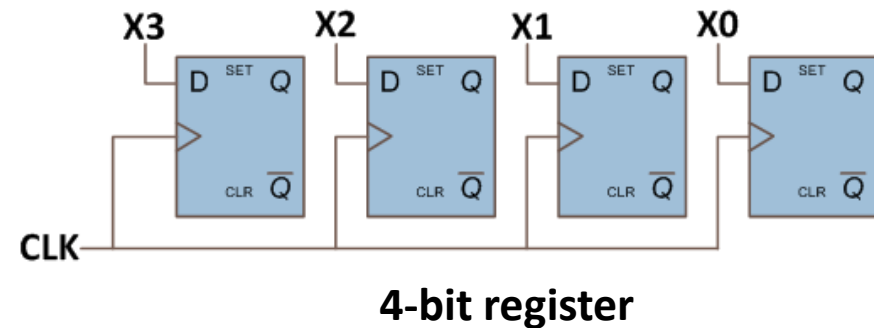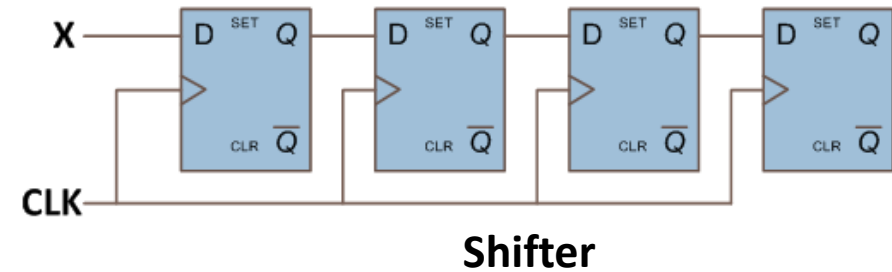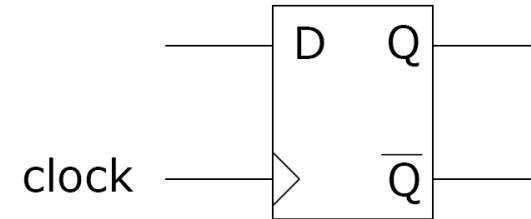



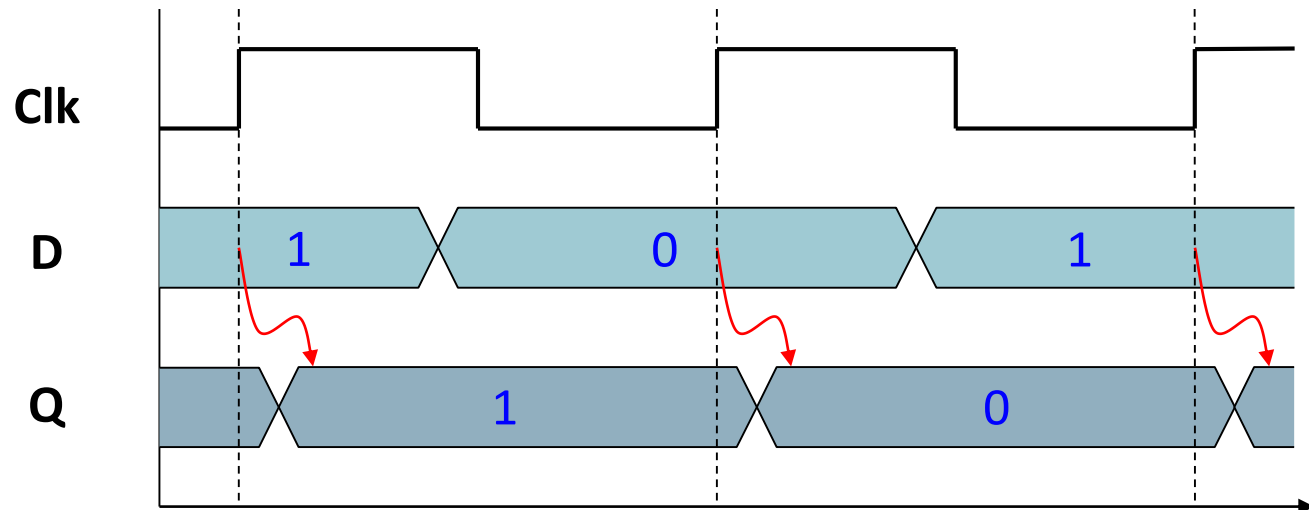
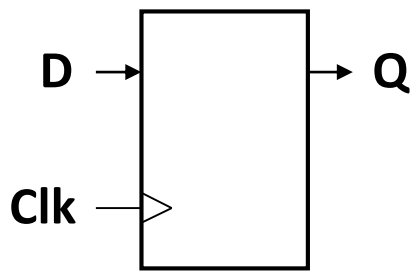
# Sequential Elements: Storing 1 bit

- Register: stores data in a circuit
  - Uses a clock signal to determine when to update the stored value
  - Edge-triggered: update when Clk changes from 0 to 1



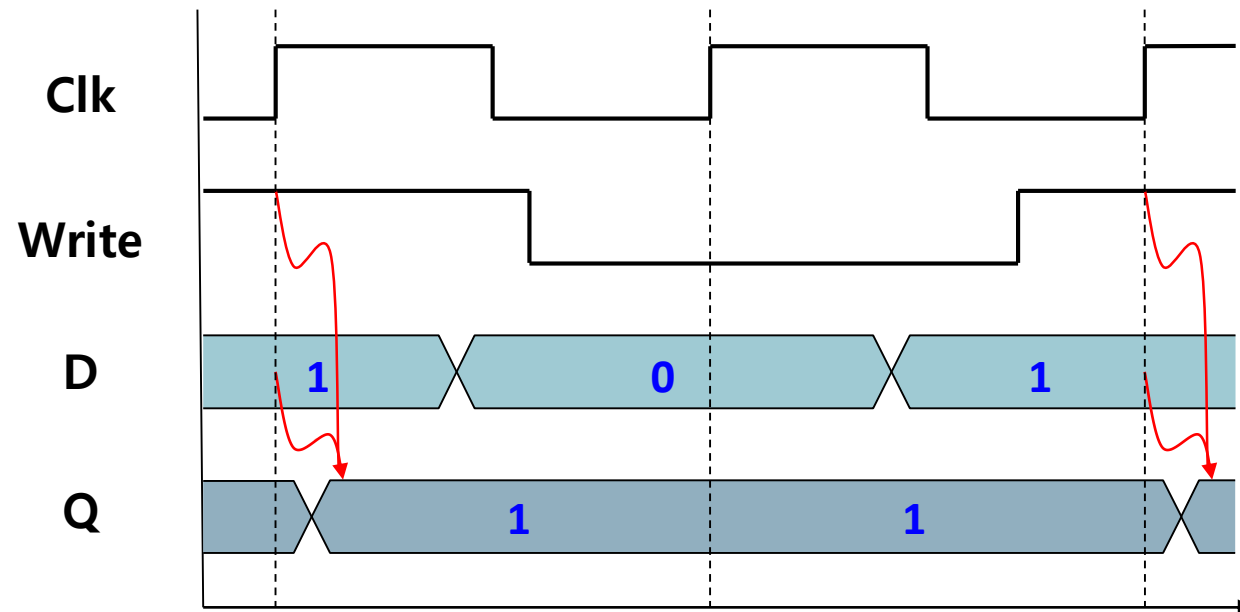
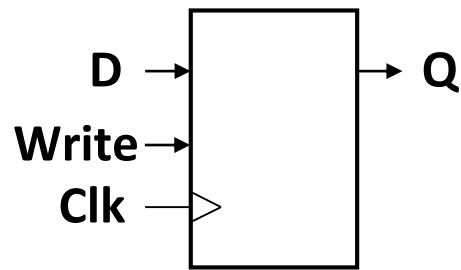
# Sequential Elements: Storing 1 bit (cont'd)

- Register with write control
  - Only updates on clock edge when write control input is 1
  - Used when stored value is required later



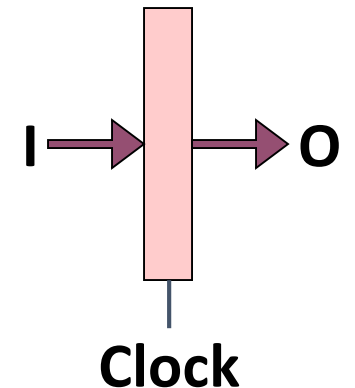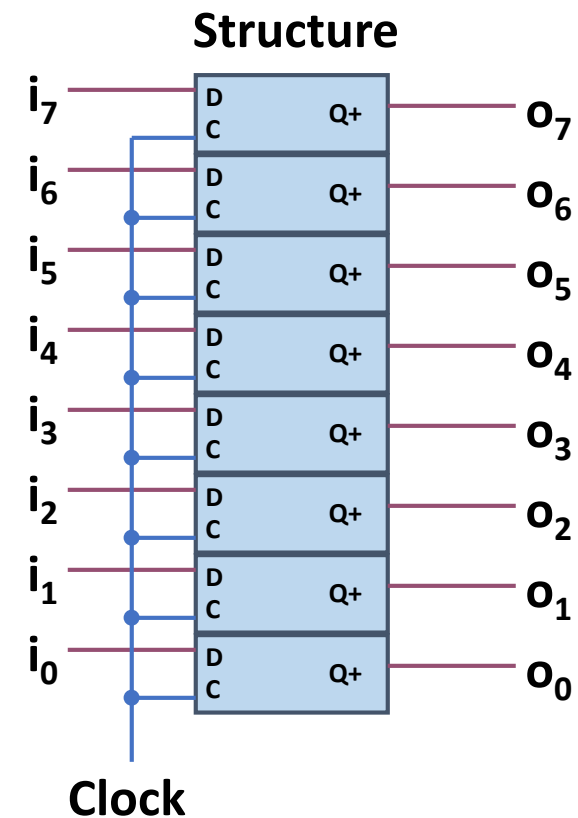
# (Hardware) Registers

- Stores word of data
  - Different from **program registers** seen in assembly code
- Collection of edge-triggered latches
- Loads input on rising edge of clock




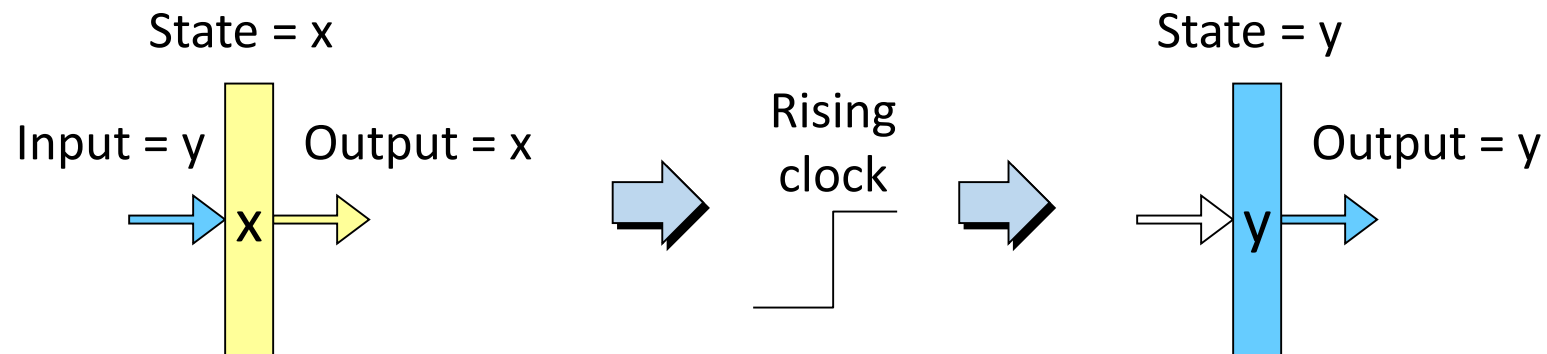
# Register Operation

- Stores data bits
- For most of time acts as barrier between input and output
- As clock rises, loads input



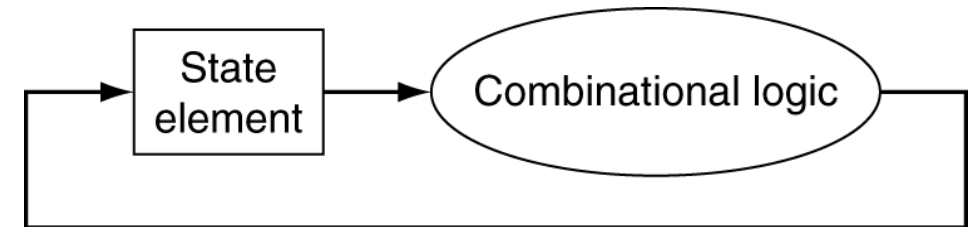
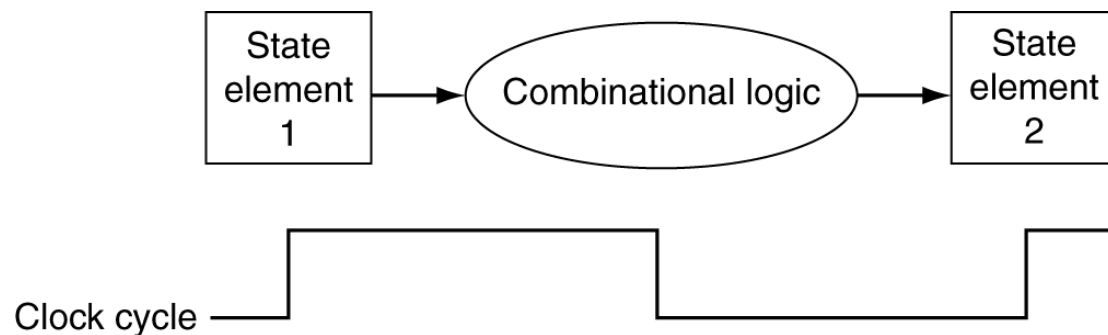
# Clocking Methodology

- **Combinational logic transforms data during clock cycles**
  - Between clock edges
  - Input from state elements, output to state element
  - Longest delay determines clock period



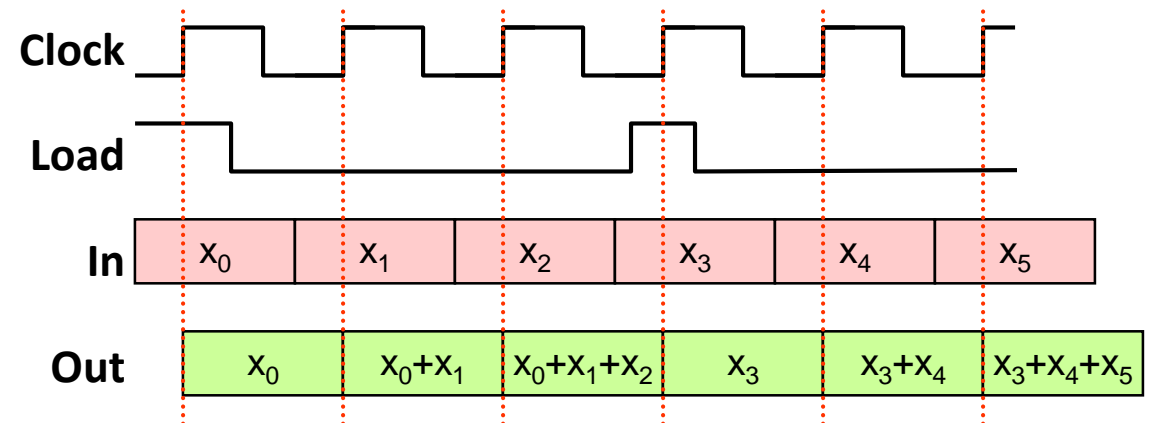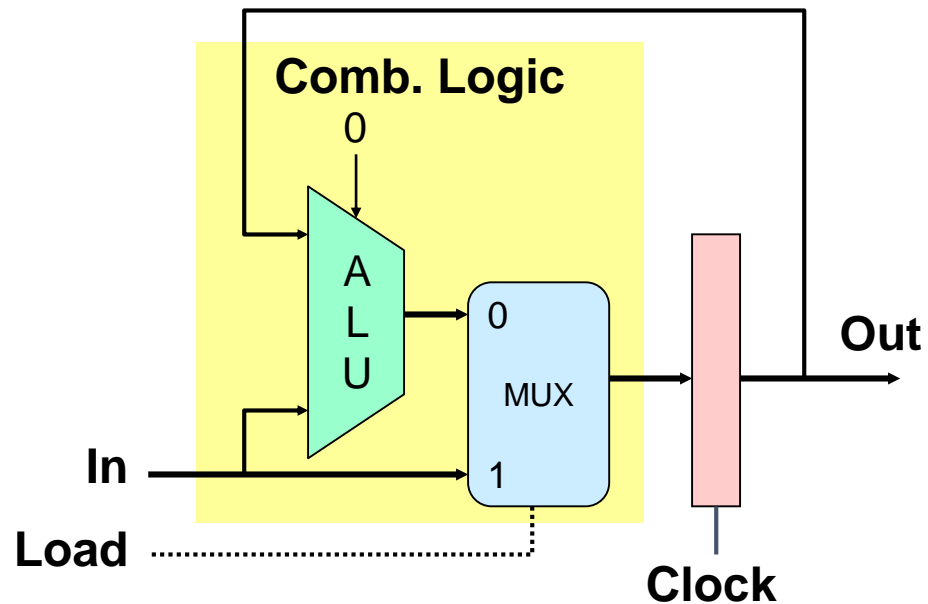
# State Machine Example

- Accumulator circuit
- Load or accumulate on each cycle


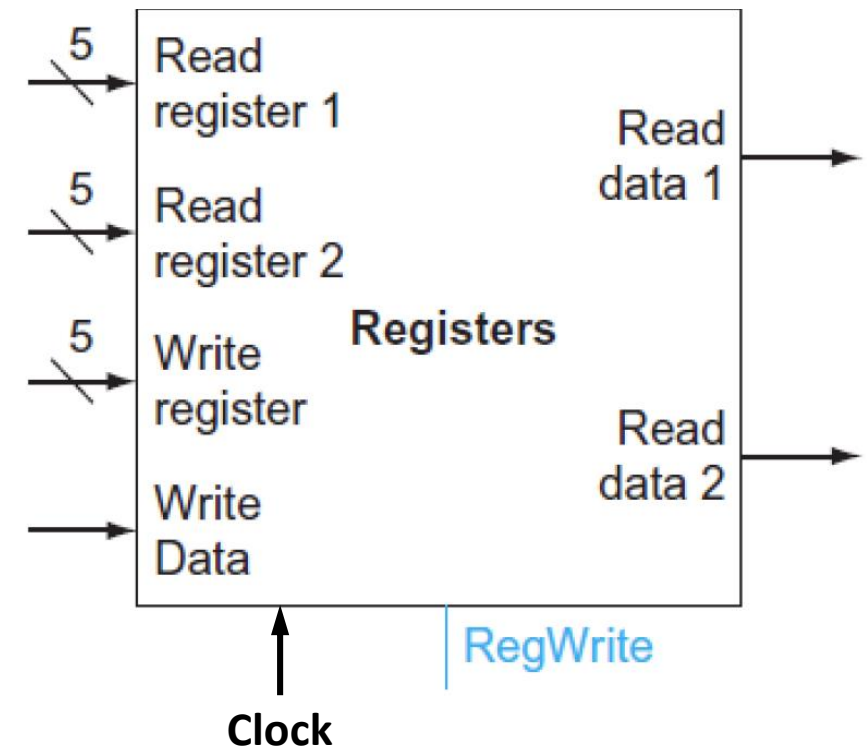
# Register File

- A collection of registers
  - Holds values of “program registers”
  - $x0 \sim x31$  in RISC-V
  - Register identifier (5 bits) serves as address
- Multiple ports
  - Can read and/or write multiple words in one cycle
  - Each has separate address and data input/output
  - Data is written to the register only when **RegWrite** signal is enabled




# Register File Timing

## ■ Reading

- Like combinational logic
- Output data generated based on input address (after some delay)
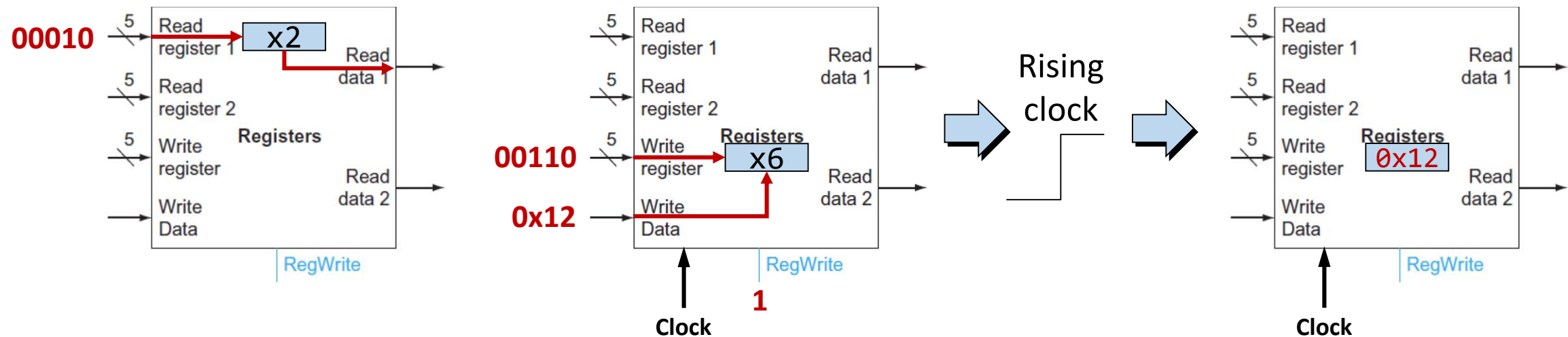
## ■ Writing


- Like register
- Update only as clock rises




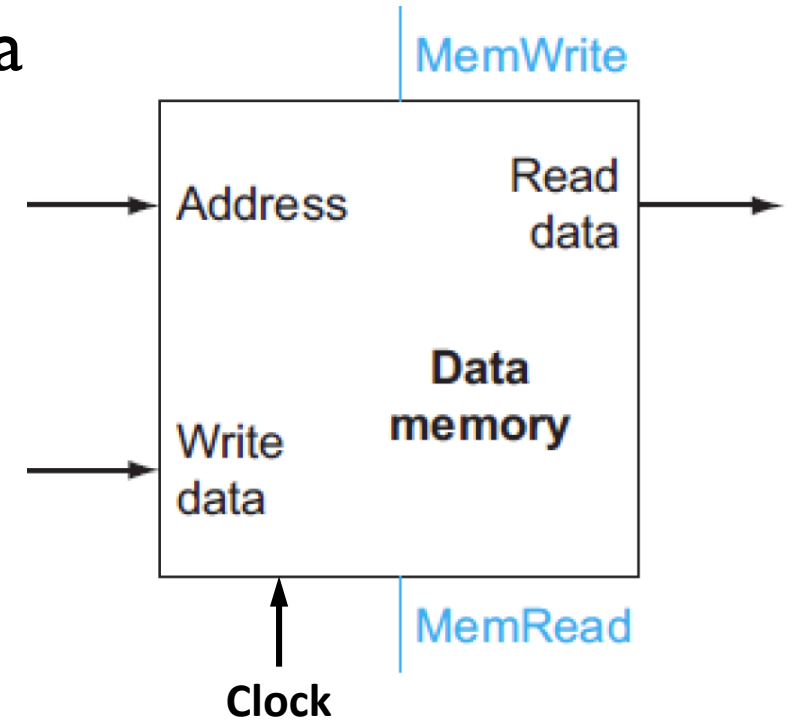
# Data Memory

- Random access memory for storing program data
- Operations similar to registers
- Reading: like combinational logic
- Writing: update only as clock rises
- Read/Write controlled using **MemWrite** and **MemRead** signals
- Another read-only memory needed for instructions
- Dual-port memory: single memory for both instructions and data
  - One read port for instructions, another read or write port for data



# Summary

## ■ Computation

- Performed by combinational logic
- Computes Boolean functions
- Continuously reacts to input changes

## ■ Storage

- Registers
  - Hold single words, Loaded as clock rises
- Random-access memories
  - Hold multiple words
  - Possibly multiple read or write ports
  - Read word when address input changes
  - Write word as clock rises

